 


---

# Types of Circuits and Diagrams



Name: \_\_\_\_\_

**Draw** the three different types of Circuits as explained in class and **label** its components  
- 3 marks

List **2 advantages** and **2 disadvantages** of each type of circuit- 3 marks

Series	
Parallel	
Combination: Series-Parallel Circuit	



---

## Types of Circuits and Diagrams

